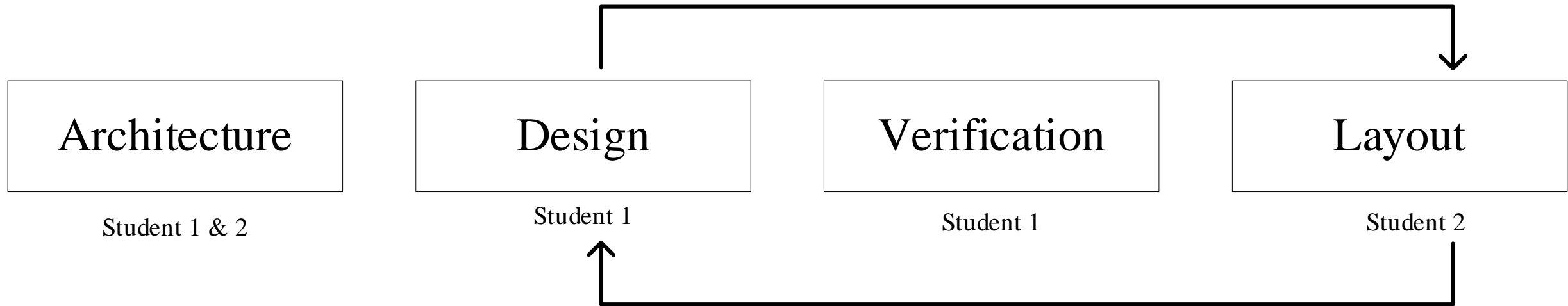


Project Guide 1

School of Information Science and
Technology
ShanghaiTech University





Recommended Division of Labor




Timing Design

  - Pulse generation based on: delay line (left) & feedback (right).
- Signal with timing information is implemented by “waveform signal AND enable signal”.





FF

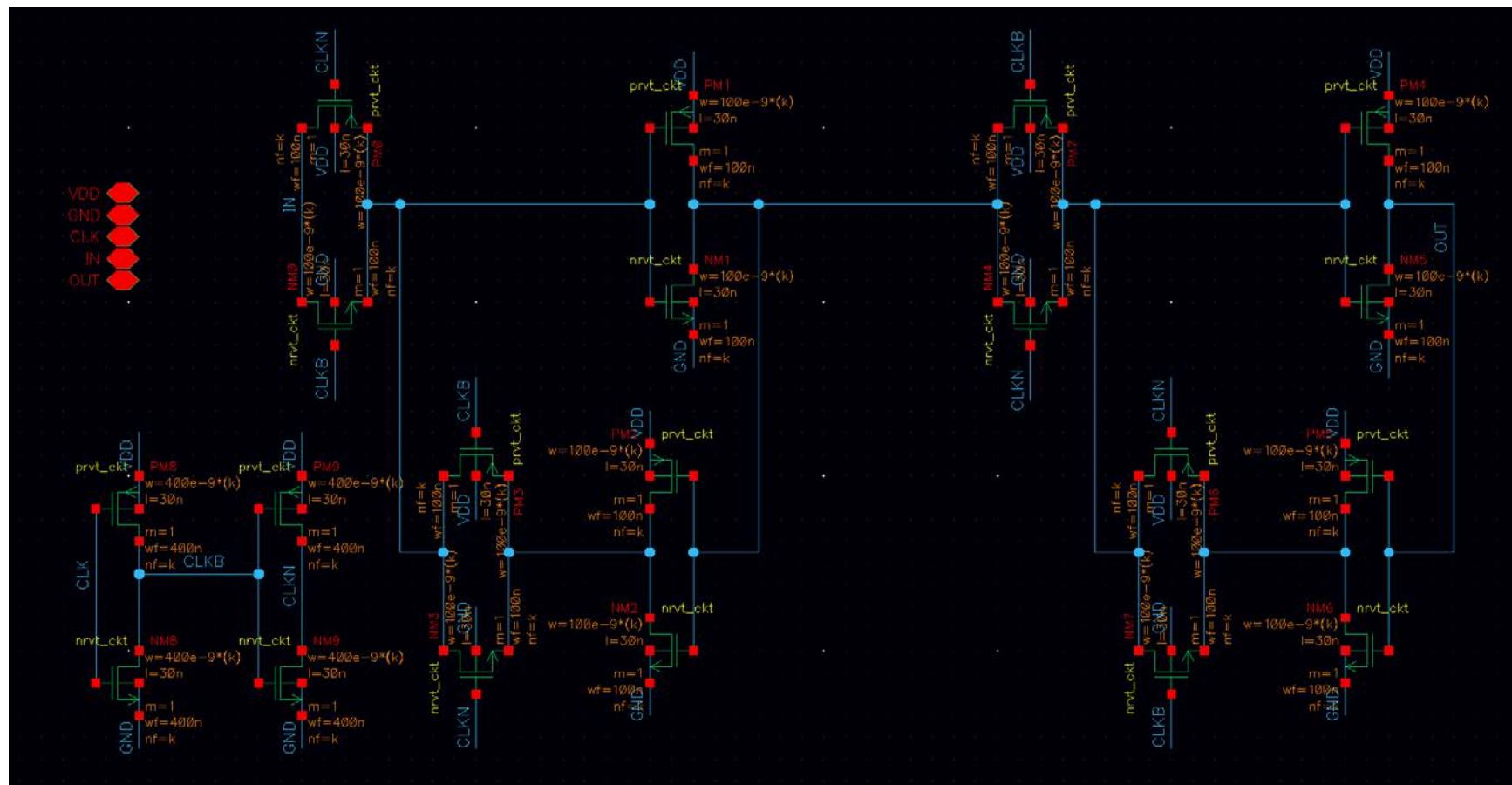


Bitcell Array with Bus

 
 
- Bitcell column (left); bitcell array (right).
- Use “shift+e” to select and plot the signal in the module.



A Pre-Simulation Example

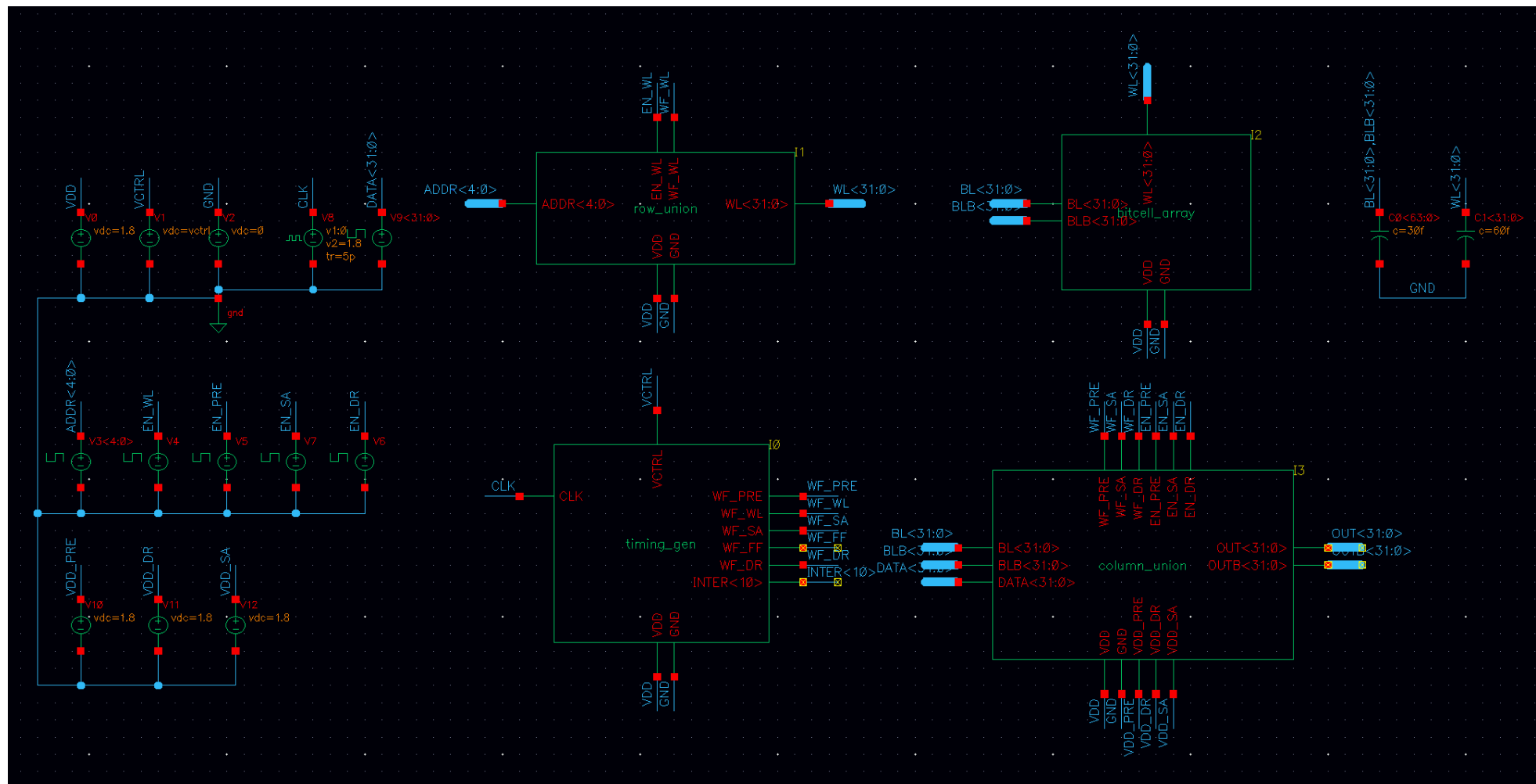

Layout with Body Tap

  

Layout with Multiple Views

- Cellview with multiple layout views (left) and with no schematic view (right).

View ▲	Lock	
layout		
layout_fig		
layout_half		
layout_half_push		
layout_lvs		
schematic		
symbol		

View ▲	Lock	
layout		

